

Audio Amplifier Project Report

Power Supply stage(stage 3)

I used a common collector with a 2N3055 transistor due to power capabilities.

$Power = V * I = (938mV) * (117 mA) = 0.1097 \text{ Watts}$. Thus the transistors doesn't exceed 250mW and it will keep it from overheating.

- $V_{RB2} = \frac{R_{B2}}{R_{B1} + R_{B2}} V_{CC} \rightarrow \frac{3.3k\Omega}{1k\Omega + 3.3k\Omega} * 5 = 3.83V$
- $V_{RE} = V_{RB2} - 0.7 \rightarrow 3.83 - 0.7 = 3.13V$
- $I_e = \frac{V_{RE}}{R_E} \approx I_C \rightarrow \frac{1V}{8} = 0.125A$


1st and 2nd Stage Calculations and Equations

Values Defined: $V_{CC} = 5V$; $V_0 = 0.5V$; $V_{CE,sat} = 0.5V$; $V_{RE} = 1V$; $V_{RC} = 2.5V$; $R_i = 50k\Omega$; and $\beta = 200$

- $V_{CC} - V_o - V_{RE} - V_{CE,sat} > V_{RC} > V_o \Rightarrow 5V - 0.5V - 1V - 0.5V > 3.0V > 0.5V$
- Stage2: $\frac{V_{RC} - 0.7 - V_o}{R_H} \geq \frac{V_o}{R_L} \Rightarrow R_H = 1,000 \text{ ohms}$, and I excluded R_L in the design
- Stage 2: $I_{C2} = \frac{V_{RC} - 0.7}{R_H} \Rightarrow I_{C2} = 2.3mA$
- Stage 2: $\frac{I_{C2}}{\beta} \leq I_{C1} \leq \frac{\beta}{R_i} \frac{1}{\frac{N}{V_{RE} + 0.7} + \frac{N}{V_{CC} - V_{RE} - 0.7} + \frac{A_V}{V_{RC}}} \Rightarrow 10 * \frac{540\mu A}{200} \leq 200\mu A \leq \frac{200}{50k\Omega} * \frac{1}{\frac{10}{1.7V} + \frac{10}{3.3V} + \frac{5}{3V}}$
- Stage 1: $I_{C1} \leq \frac{\beta}{R_i} \frac{1}{\frac{N}{V_{RE} + 0.7} + \frac{N}{V_{CC} - V_{RE} - 0.7} + \frac{A_V}{V_{RC}}} \Rightarrow 300\mu A \leq \frac{200}{50k\Omega} * \frac{1}{\frac{10}{1.7V} + \frac{10}{3.3V} + \frac{5}{3V}}$
- Stage 2: $R_c = \frac{3V}{200\mu A} = 15k\Omega$; $R_E = \frac{1V}{200\mu A} = 5k\Omega$; $R_g = \frac{15k\Omega}{5} - \frac{0.025}{200\mu A} = 2.8k$; $R_{B1} = \frac{200 * (3.3V)}{10(200\mu A)} = 165k\Omega$; $R_{B2} = \frac{200(1.7V)}{10 * 200\mu A} = 85$
- Stage 1: $R_c = \frac{3V}{300\mu A} = 10k\Omega$; $R_E = \frac{1V}{300\mu A} = 3.3k\Omega$; $R_g = \frac{150\Omega}{5} - \frac{0.025}{300\mu A} = 2k\Omega$; $R_{B1} = \frac{200 * (3.3V)}{10(300\mu A)} = 220k\Omega$; $R_{B2} = \frac{200(1.7V)}{10 * 300\mu A} = 1$

$Av = Av_1 * Av_2 * Av_3 = 5 * 5 * 1 = 25 \text{ gain}$ NOTE: resistor values adjusted in measurement to to attain a gain of 25

Figure A: Audio Amplifier Schematic with Interactive Points

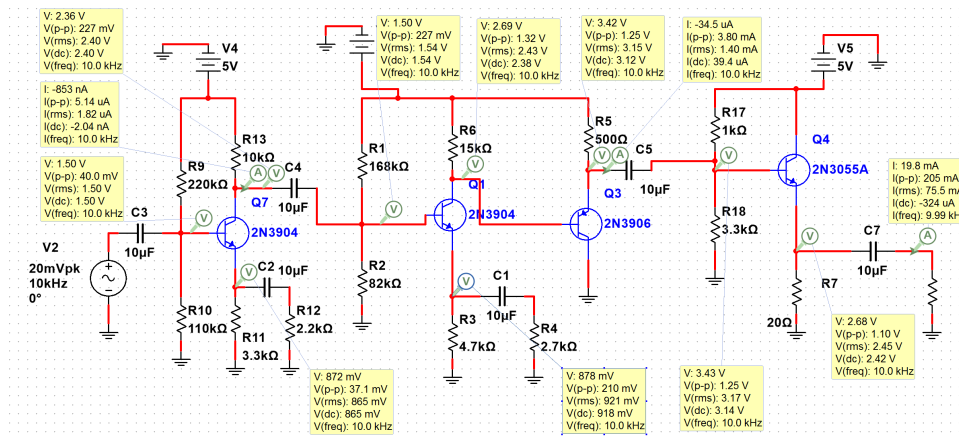

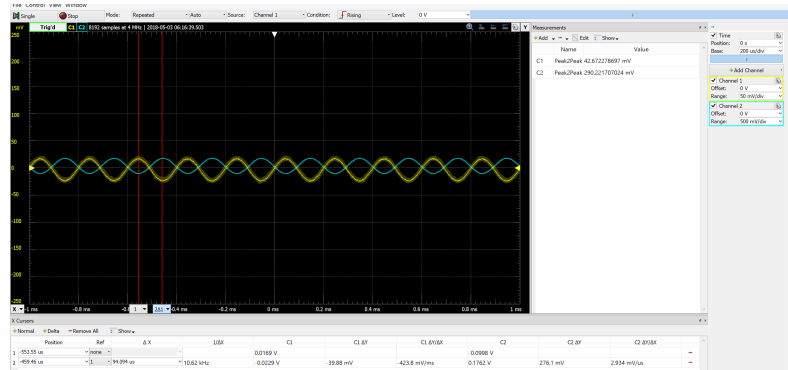


Figure 2: Stage 2 Transient Waveform with 20mV

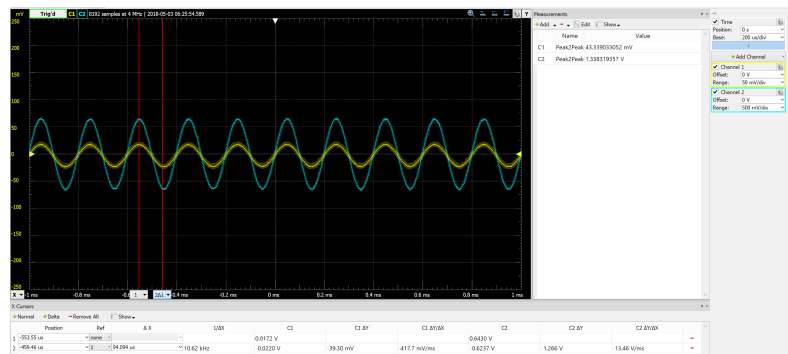


Figure 3: AC Frequency Response Stage 3

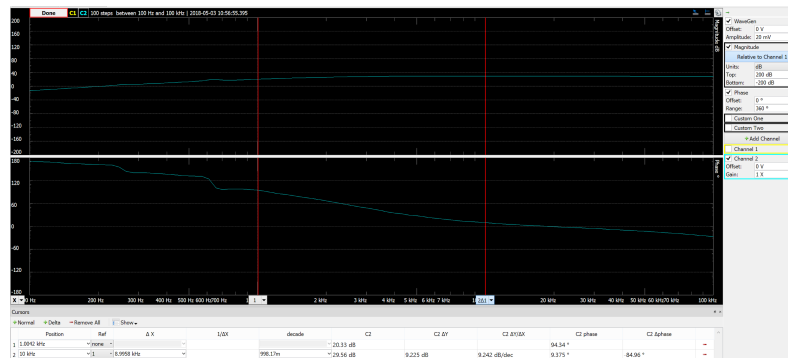


Figure 5: Transient Response Stage 3 with 10 mV

Figure 5: Transient Response Stage 3 with 20mV

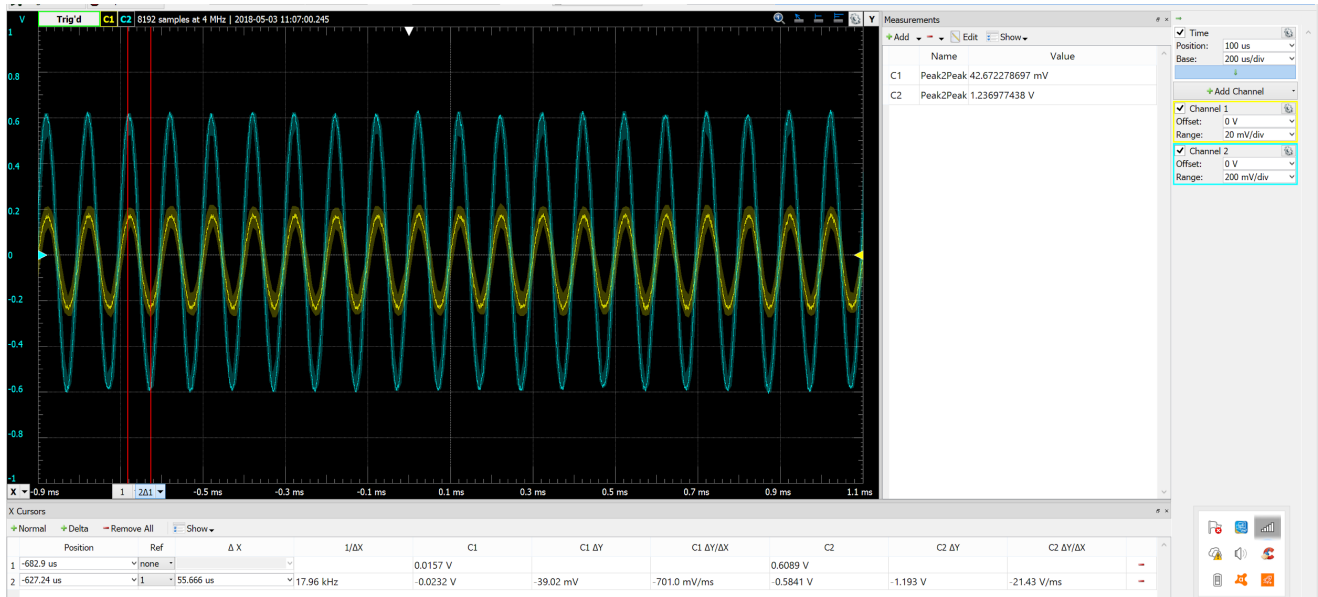


Figure 6: Transient Response Stage 3 with 30mV

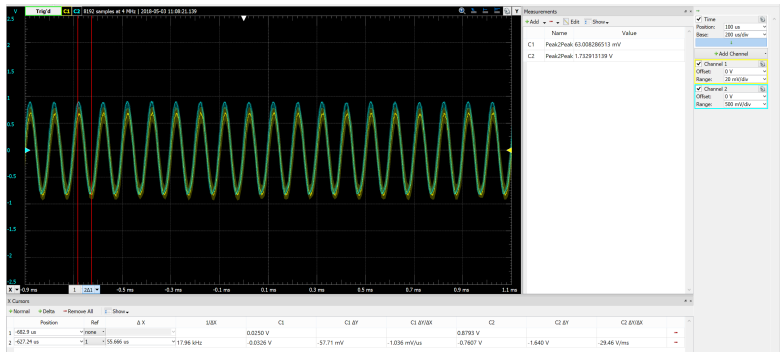


Figure 7: Transient Response Stage Stage 3 with 40mV

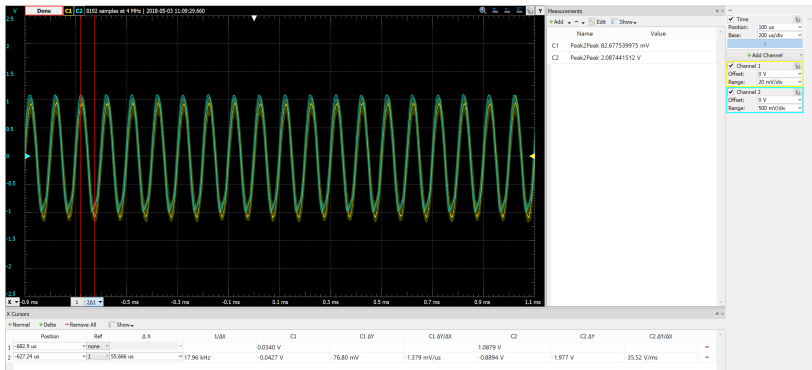


Figure 6: Total Harmonic Distortion at Stage 2

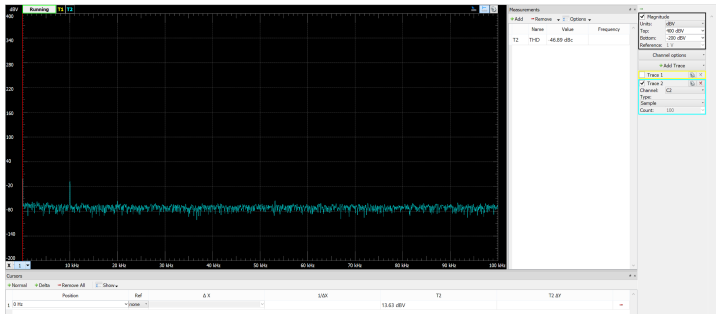


Figure 7: Total Harmonic Distortion at Stage 3

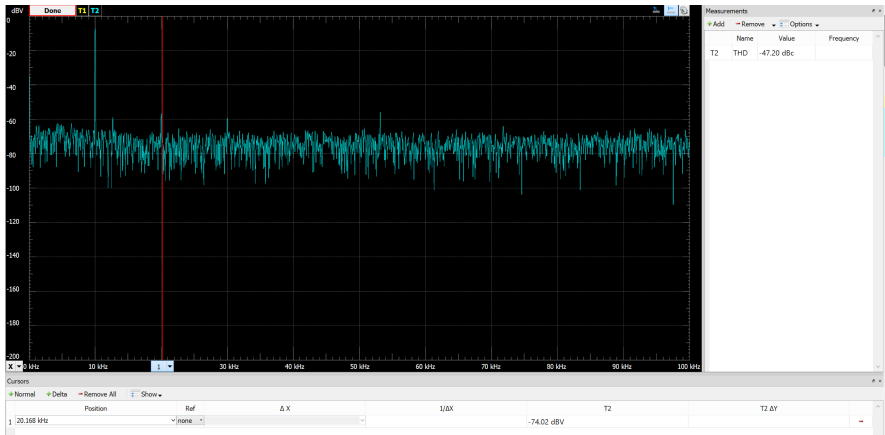


Table 1: DC Operating Points at every stage

Stage 1		Stage 2(@ pnp)		Stage 3	
Vbase	1.41V	Vbase	1.937 V	Vbase	3.365 V
Vcollector	2.242 V	Vcollector	2.623 V	Vcollector	5V

Vemitter	878 mV	Vemitter	20mV	Vemitter	2.733 V
----------	--------	----------	------	----------	---------

Discussion:

On the power amplifier, I used a 2N3055 Transistor, since the power capabilities of this transistor is greater than a 2N3904 transistor. Then I constructed a common collector with emitter follower as shown in lab 08 with $R_b=825\Omega$ and $R_E=20\Omega$ in parrell with $R_L=8\Omega$. The second stage, I used lab manual 09 to construct a common emitter followed with a buffer. The gain for this stage was gain of 4.23 and with previous stage it totaled to a gain of 27.5 ($AV=AV_1*AV_2*AV_3=4*6.5*1=27.5$). Therefore, the output at the second stage is approximately 1.1V. Then, the first stage, I used a common emitter with a gain of 6.5 and the input resistance was 50k with a low total harmonic distortion. For the first two stages in my design I had to adjust the swing to 0.5 V with $V_{re}=1$ V and $V_{rc}=3$ V. Then, I proceed the calculations as demonstrated in lab manual 08 and 09. I adjusted a couple resistor values(mainly R_g and R_h) to fit with my measurement circuit model. Then, a link to the video results will be attached to demonstrate my results and lab performance.

<https://www.youtube.com/playlist?list=PLWMKE8Zrb39ZpDBgFhjb1N-XxiXJWxDpn>